

EC 551 – Advanced Digital Design with Verilog and FPGAs

Lecture 2 Combinational Logic Review


Prof. Douglas Densmore

Announcements



- Don't forget that the "Syllabus Confirmation" is due **Tuesday (9/15) in class.**
- Make sure you have access to Blackboard (you need it to get the syllabus confirmation). I don't want to hear about issues midway through the semester.
- Also make sure to sign up for Piazza - piazza.com/bu/fall2026/engec551
- "Quiz" sheets available on Blackboard. We will do them in class on (9/15). **Do them BEFORE class!**

Read Chapter 2 Advanced Digital Design
with the Verilog HDL (2nd Edition)


CMOS Gates

 

x	y	F
0	0	0
0	1	1
1	0	1
1	1	1

  


When an input is 1

 



When both inputs are 0




CMOS Gates

 

x	y	F
0	0	0
0	1	0
1	0	0
1	1	1

  

When both inputs are 1

 

When an input is 0



CMOS Logic

- What was “wrong” with the circuits previously shown from an actual VLSI implementation standpoint?
- How do you “chain” circuits together?
- What are some issues when creating “long chains”? What is this called?

Boolean Algebra Intro

- Developed mid-1800's by George Boole to formalize human thought
 - Ex: "I'll go to lunch if Mary goes OR John goes, AND Sally does not go."
 - Let F represent my going to lunch (1 means I go, 0 I don't go)
 - Likewise, m for Mary going, j for John, and s for Sally
 - Then **$F = (m \text{ OR } j) \text{ AND NOT}(s)$**
 - Nice features
 - Formally evaluate
 - $m=1, j=0, s=1 \rightarrow F = (1 \text{ OR } 0) \text{ AND NOT}(1) = 1 \text{ AND } 0 = \underline{0}$
 - Formally transform
 - $F = (m \text{ and NOT}(s)) \text{ OR } (j \text{ and NOT}(s))$
 - » Looks different, but same function
 - » We'll show transformation techniques soon
 - Formally prove
 - Prove that if Sally goes to lunch ($s=1$), then I don't go ($F=0$)
 - $F = (m \text{ OR } j) \text{ AND NOT}(1) = (m \text{ OR } j) \text{ AND } 0 = 0$

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

a	NOT
0	1
1	0

Boolean Algebra 1

- Commutative
 - $a + b = b + a$
 - $a * b = b * a$
- Distributive
 - $a * (b + c) = a * b + a * c$
 - Can write as: $a(b+c) = ab + ac$
 - $a + (b * c) = (a + b) * (a + c)$
 - (This second one is tricky!)
 - Can write as: $a+(bc) = (a+b)(a+c)$
- Associative
 - $(a + b) + c = a + (b + c)$
 - $(a * b) * c = a * (b * c)$
- Identity
 - $0 + a = a + 0 = a$
 - $1 * a = a * 1 = a$
- Complement
 - $a + a' = 1$
 - $a * a' = 0$
- To prove, just evaluate all possibilities

Example uses of the properties

- Show abc' equivalent to $c'ba$.
 - Use commutative property:
 - $a*b*c' = a*c'*b = c'*a*b = c'*b*a$
- Show $abc + abc' = ab$.
 - Use first distributive property
 - $abc + abc' = ab(c+c')$.
 - Complement property
 - Replace $c+c'$ by 1: $ab(c+c') = ab(1)$.
 - Identity property
 - $ab(1) = ab*1 = ab$.
- Show $x + x'z$ equivalent to $x + z$.
 - Second distributive property
 - Replace $x+x'z$ by $(x+x')*(x+z)$.
 - Complement property
 - Replace $(x+x')$ by 1,
 - Identity property
 - replace $1*(x+z)$ by $x+z$.



Boolean Algebra 2

- Null elements
 - $a + 1 = 1$ (Unit property)
 - $a * 0 = 0$ (Zero property)
- Idempotent Law
 - $a + a = a$
 - $a * a = a$
- Involution Law
 - $(a')' = a$
- DeMorgan's Law
 - $(a + b)' = a'b'$
 - $(ab)' = a' + b'$
 - *Very useful!*
- To prove, just evaluate all possibilities
- Absorption
 - $a + ab = a$
 - $a(a+b) = a$
- Consensus
 - $ab + bc + a'c = ab + a'c$
 - $(a+b)(b+c)(a'+c) = (a+b)(a'+c)$



SOP

- Truth tables too big for numerous inputs
- Use standard form of equation instead
 - Known as *canonical form*
 - Regular algebra: group terms of polynomial by power
 - $ax^2 + bx + c$ ($3x^2 + 4x + 2x^2 + 3 + 1 \rightarrow 5x^2 + 4x + 4$)
 - Boolean algebra: create sum of minterms
 - **Minterm**: product term with every function literal appearing exactly once, in true or complemented form
 - Just multiply-out equation until sum of product terms
 - Then expand each term until all terms are minterms

Q: Determine if $F(a,b)=ab+a'$ is equivalent to $F(a,b)=a'b'+a'b+ab$, by converting first equation to canonical form (second already is)

$F = ab+a'$ (already sum of products)


$F = ab + a'(b+b')$ (expanding term)

$F = ab + a'b + a'b'$ (Equivalent – same three terms as other equation)





K-Maps 1

- Easy to miss possible opportunities to combine terms when doing algebraically
- **Karnaugh Maps (K-maps)**
 - **Graphical** method to help us find opportunities to combine terms
 - Minterms differing in one variable are *adjacent* in the map
 - Can clearly see opportunities to combine terms – look for adjacent 1s
 - For F, clearly two opportunities
 - Top left circle is *shorthand* for:
 $x'y'z' + x'y'z = x'y'(z' + z) = x'y'(1) = x'y'$
 - Draw circle, write term that has all the literals except the one that changes in the circle
 - Circle xy, x=1 & y=1 in both cells of the circle, but z changes (z=1 in one cell, 0 in the other)
 - Minimized function: OR the final terms

 

$$F = x'y'z + xyz + xyz' + x'y'z'$$

  

$$F = x'y' + xy$$

$$\begin{aligned} F &= xyz + xyz' + x'y'z' + x'y'z \\ F &= xy(z + z') + x'y'(z + z') \\ F &= xy*1 + x'y'*1 \\ F &= xy + x'y' \end{aligned}$$

Easier than algebraically:



K-Maps 2

General K-map method

1. *Convert* the function's equation into sum-of-minterms form
2. *Place* 1s in the appropriate K-map cells for each minterm
3. *Cover* all 1s by drawing the fewest largest circles, with every 1 included at least once; write the corresponding term for each circle
4. *OR* all the resulting terms to create the minimized function.


Example: Minimize:

$$G = a + a'b'c' + b'(c' + bc')$$


1. Convert to sum-of-products

$$G = a + a'b'c' + bc' + bc'$$

2. Place 1s in appropriate cells

 

3. Cover 1s

 

4. OR terms: $G = a + c'$



Glitches and Hazards 1

- **Glitch**: Unwanted switching at the outputs
- **Hazard**: Component organization which causes glitch
- Occur when different paths through circuit have different propagation delays
- Dangerous if logic causes an action while output is unstable
 - may need to guarantee absence of glitches



AB \ CD		A			
		00	01	11	10
00		0	0	1	1
01		1	1	1	1
11		1	1	0	0
10		0	0	0	0

Prime implicants are highlighted with red boxes: $\overline{A}C$ (top-left 2x2), $\overline{A}D$ (top-right 2x2), and AB (middle-left 2x2). A red arrow points from the $\overline{A}D$ group to the AB group.

$$F = A\overline{C} + \overline{A}D$$

When the input change by a **single** bit from 1101 to 0101,
When A goes low A' goes high
after an inverter delay and a glitch has happened



The input change spans prime implicants

  

Tabular Method Step 1: Determine Prime Implicants

  - Example function: $F = x'y'z' + x'y'z + x'yz + xy'z + xyz' + xyz$

Actually, comparing ALL pairs isn't necessary—just pairs differing in uncomplemented literals by one.



↑
Implicant's number of uncomplemented literals

Prime implicants:

$x'y'$ xy z



Tabular Method Step 2: Add Essential PIs to Cover

- Prime implicants (from Step 1): $x'y'$, xy , z

Prime implicants

Minterms	$x'y'$ (0,1)	xy (6,7)	z (1,3,5,7)
(0) $x'y'z'$	X		
(1) $x'y'z$	X		X
(3) $x'yz$			X
(5) $xy'z$			X
(6) xyz'		X	
(7) xyz		X	X

(a)

Prime implicants

Minterms	$x'y'$ (0,1)	xy (6,7)	z (1,3,5,7)
(0) $x'y'z'$	X		
(1) $x'y'z$	X		X
(3) $x'yz$			X
(5) $xy'z$			X
(6) xyz'		X	
(7) xyz		X	X

(b)

Prime implicants

Minterms	$x'y'$ (0,1)	xy (6,7)	z (1,3,5,7)
(0) $x'y'z'$	X		
(1) $x'y'z$	X		X
(3) $x'yz$			X
(5) $xy'z$			X
(6) xyz'		X	
(7) xyz		X	X

(c)

If only one X in row, then that PI is essential—it's the only PI that covers that row's minterm.



Next Time

- Sequential Logic Review
- Be sure to get the Combinational Logic Review “Quiz” from Blackboard

Questions?