Shani "Dill" De Silva
U14033199

(3B) If all LUTs had to be 4-input functions & all line-line connections could be made:

My gate:
- 7 LUTs used.
- 15 horizontal lines used
- 2 vertical lines used (inter-LUT columns)

However! Assuming Question means ~~[illegible]~~ value of SRAM needed to store function/connection when gates fully used:

(if) 16 bits per 4 input LUT.

(if) 12 total LUTs

(if) vertical/horizontal wire intersections are governed by switch box matrix.

For 12 LUTs with 4 inputs = 192 bits. storage.
↳ 16 bits to store answers

Routing wires: 32 horizontal, 24 vertical, $32 \times 24 = 768$ bits

5 pins on each LUT, 12 LUTs: 60 connections to wires.

however! 8 options each $(8 \times 4 + 8)12 = 480$ bits.
(40×12)



$\geq$

12 LUTs x 5 Pins x 8 options per pin.

$12 \times 40 = 480$.

$192 + 768 + 480 = 1440$ bits